

CPSC 1000: Introduction to Computer Science

Week 2: generating digital signals

Robert Benkoczi, C556
`robert.benkoczi@uleth.ca`

18-Sep-2018

Week 1 lecture objectives


To prepare students for lab activity 1: Arduino's digital output. Digital output is needed for the functioning of various electronic components, such as the ultrasonic distance sensor.

- ▶ Students will examine the different pins of an Arduino micro-controller.
- ▶ Students will write a simple program for the Arduino to generate a digital signal.
- ▶ Students will assemble a simple electronic circuit using a breadboard to visualize the digital signal.

An Arduino and its pins

Digital signal { signal that represents binary info { 0
Voltage at a pin of the Arduino { 5V : bit 1
0V : bit 0
digital pins

 → when appropriately configured, digital pins on the Arduino can behave like a battery that can be turned on → bit 1
off → bit 0





Breadboard

Hobbyists used breadboards to test electronic circuit prototypes.






The breadboard we will use

  


Example

Connect two resistors in parallel

   

 
Exercises

- ▶ Two resistors in series.
- ▶ Two resistors in parallel, connected in series with one resistor.
- ▶ Two parallel resistors in series with other two parallel resistors.
- ▶ Two series resistors, in parallel with other two series resistors.



==


series
connection.

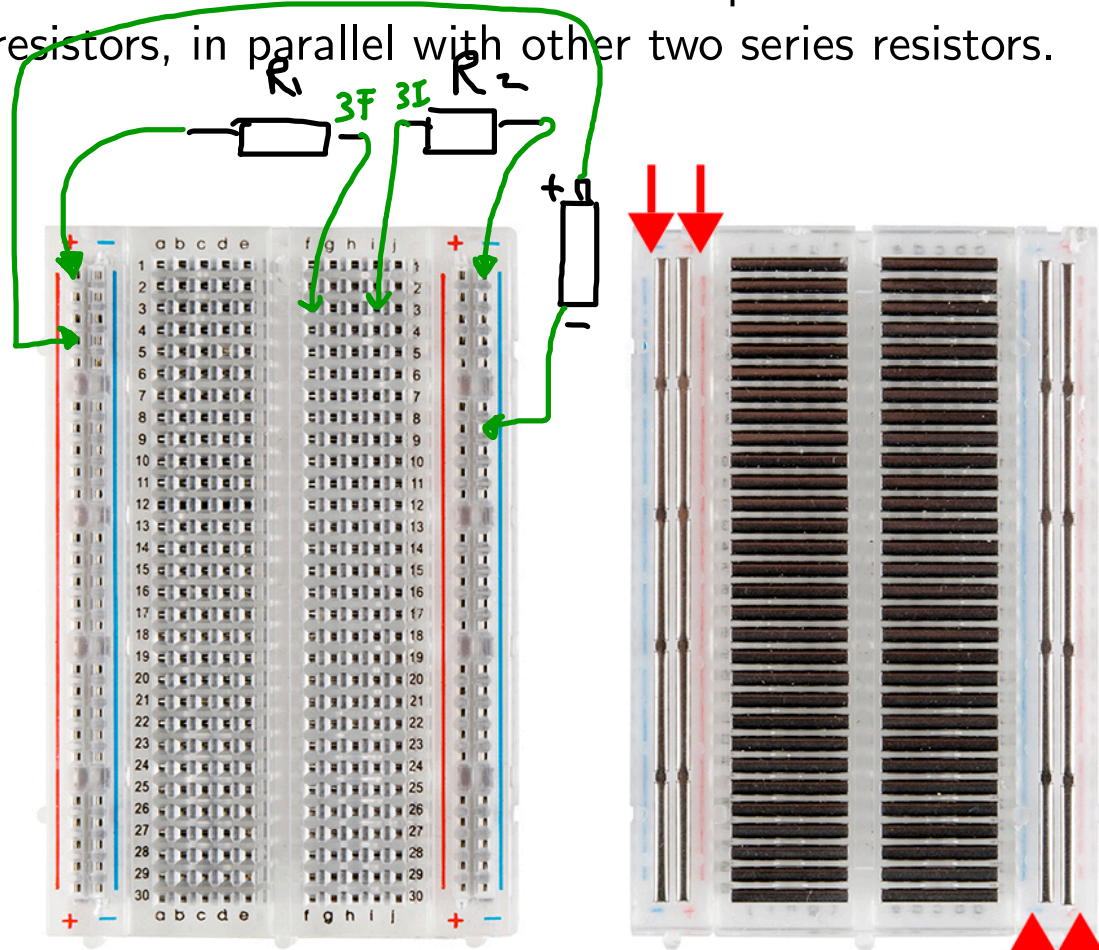

Diodes


- ▶ Current flows only in one direction (in the opposite direction the current is very small, "reverse current").
- ▶ There is voltage in the forward direction, "forward voltage".
- ▶ There is a max current in forward direction (higher current can damage the LED) I_{max} .
- ▶ There is a max voltage in the reverse direction, "breakdown voltage". (V_{min}).

 Lab objective: use an inexpensive component (LED) to "see" the digital signal generated.



Using an LED with the arduino, Ohm,'s Law

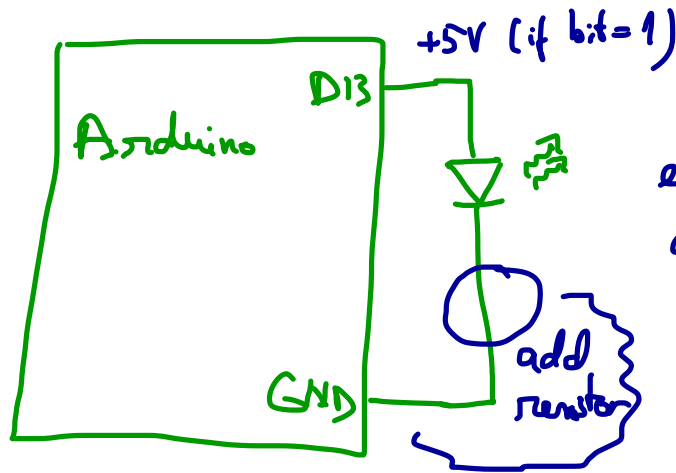- ▶ Max current out of an Arduino's digital pin: 40 mA (also note the LED's max forward current).
- ▶ Bit 1 represented as +5 V.
- ▶ Forward voltage on a LED, eg: 2.5 V.
- ▶ $U = I \cdot R$, I : current (intensity), R : resistance, U : voltage.




← at 5V, the only electrical resistance will be given by circuits inside Arduino (LED: completely open)
The current will be $\gg 40 \text{ mA}$.

⇒ We can use a resistor to "slow down" the current.

Diagram (upgraded)

When Arduino outputs a "1" on D13

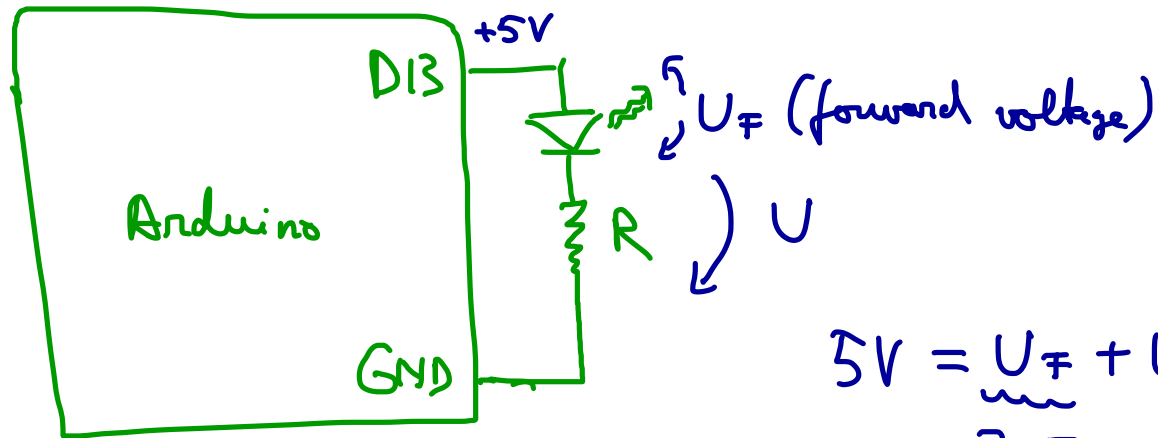

$$5V = \underbrace{U_F}_{2.5} + U \quad U \approx 2.5$$

Say our target is a current of around 10mA ($\frac{1}{4} \times \text{max current}$) to be safe, then what value of R do we need?

$$\underline{\underline{U}} = R \cdot \underline{\underline{I}}$$

$2.5 \quad 10\text{mA} = 10 \cdot 10^{-3} \text{A}$

$$R = \frac{U}{I} \approx \frac{2.5}{10 \cdot 10^{-3}} = 250 \Omega$$

The lab uses 220Ω

Programming the Arduino to generate digital signals

Digital signal:

- ▶ 0V = bit 0
- ▶ 5V = bit 1.

Arduino digital pins:

- 2 modes {
- ▶ Input = measuring device
 - ▶ Output = battery

Step 1 : make sure the digital pin we want to use is in "output" mode

Step 2 : output a "1" or "0" on that pin.

Setting up the digital pin for input/output

Function pinMode:

Example:

```
void setup()  
{  
  pinMode(13, OUTPUT);  
}
```

← function call

↑
argument 1:
pin number
that we configure

↑
argument 2:
the mode

OUTPUT: integer variable
with a predefined
value.

HINT: Find out what
value OUTPUT is.
Compare this with
the value for INPUT

Generating bit 1 or bit 0

Function digitalWrite

Example:

```
void loop()
{
  digitalWrite(13, HIGH);
  delay(1000); // Wait for 1000 millisecond(s)
  digitalWrite(13, LOW);
  delay(1000); // Wait for 1000 millisecond(s)
}
```


pin number
↑
value of the bit
1 (HIGH)
0 (LOW)

HIGH, LOW are also predefined integer variables
(find out their values)

} blinking pattern
(1 sec on / 1 sec. off)

Make the LED blink twice in a second

 
Keeping the circuit, we will change the code to solve this problem.



blink blink

```
void loop() {  
  digitalWrite(13, HIGH);  
  delay(250);  
  digitalWrite(13, LOW);  
  delay(250);  
}
```

 Program a long blink followed by a short blink



```
void loop() {
    digitalWrite(13, HIGH);
    delay(500);
    digitalWrite(13, LOW);
    delay(300);
    ...
}
```

3